NEC 304

STLD

Lecture 9

More Karnaugh Maps and Don't Cares

Rajeev Pandey Department Of ECE rajeevvce2007@gmail.com

Overview

° Karnaugh maps with four inputs

- Same basic rules as three input K-maps
- ° Understanding prime implicants
 - Related to minterms
- ° Covering all implicants
- ° Using Don't Cares to simplify functions
 - Don't care outputs are undefined
- ° Summarizing Karnaugh maps

Karnaugh Maps for Four Input Functions

- Represent functions of 4 inputs with 16 minterms
- [°] Use same rules developed for 3-input functions
- [°] Note bracketed sections shown in example.



Fig. 3-8 Four-variable Map

Karnaugh map: 4-variable example

° F(A,B,C,D) = Σm(0,2,3,5,6,7,8,10,11,14,15) F =

C + A'BD + B'D'





Solution set can be considered as a coordinate System!

Design examples



K-map for LT

K-map for EQ

K-map for GT

- LT = A'B'D + A'C + B'CD
- EQ = A'B'C'D' + A'BC'D + ABCD + AB'CD'
- GT = B C' D' + A C' + A B D'

Can you draw the truth table for these examples?

Physical Implementation



- ° Step 1: Truth table
- ° Step 2: K-map
- ^o Step 3: Minimized sum-ofproducts
- [°] Step 4: Physical implementation with gates



K-map for EQ

Karnaugh Maps

° Four variable maps.



 $^{\circ}$ Need to make sure all 1's are covered

 $^{\circ}$ Try to minimize total product terms.

 $^{\circ}$ Design could be implemented using NANDs and NORs

Karnaugh maps: Don't cares

- ° In some cases, outputs are undefined
- $^\circ~$ We "don't care" if the logic produces a 0 or a 1
- $^{\circ}$ This knowledge can be used to simplify functions.



- Treat X's like either 1's or 0's
- Very useful
- OK to leave some X's uncovered

Karnaugh maps: Don't cares

- ° $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$
 - without don't cares

A'D + C'D

- f =



Δ	B	С	D	f
0	0	0	0	0
Ō	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	X
1	1	0	1	X
1	1	1	0	0
1	1	1	1	0

Don't Care Conditions

- In some situations, we don't care about the value of a function for certain combinations of the variables.
 - these combinations may be impossible in certain contexts
 - or the value of the function may not matter in when the combinations occur
- ° In such situations we say the function is *incompletely specified* and there are multiple (completely specified) logic functions that can be used in the design.
 - so we can select a function that gives the simplest circuit
- [°] When constructing the terms in the simplification procedure, we can choose to either cover or not cover the don't care conditions.

Map Simplification with Don't Cares



° Alternative covering.



Karnaugh maps: don't cares (cont'd)

- ° $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$
 - f = A'D + B'C'D
 - f =

without don't cares with don't cares

A'D+ C'D



by using don't care as a "1" a 2-cube can be formed rather than a 1-cube to cover this node

don't cares can be treated as 1s or 0s depending on which is more advantageous

Definition of terms for two-level simplification

° Implicant

• Single product term of the ON-set (terms that create a logic 1)

° Prime implicant

• Implicant that can't be combined with another to form an implicant with fewer literals.

° Essential prime implicant

- Prime implicant is essential if it alone covers a minterm in the K-map
- Remember that all squares marked with 1 must be covered

[°] Objective:

- Grow implicant into prime implicants (minimize literals per term)
- Cover the K-map with as few prime implicants as possible (minimize number of product terms)

Examples to illustrate terms





В

minimum cover: 4 essential implicants

Any single 1 or group of 1s in the Karnaugh map of a function F is an implicant of F.

A product term is called a prime implicant of F if it cannot be combined with another term to eliminate a variable.



If a function F is represented by this Karnaugh Map. Which of the following terms are implicants of F, and which ones are prime implicants of F?

- (a) AC'D' (b) BD (c) A'B'C'D' (d) AC'
 - (u) AC (e) B'C'D'

Implicants: (a),(c),(d),(e)

Prime Implicants: (d),(e)

Essential Prime Implicants

A product term is an essential prime implicant if there is a minterm that is only covered by that prime implicant.

- The minimal sum-of-products form of F must include all the essential prime implicants of F.



Fig. 3-11 Simplification Using Prime Implicants

Summary

- ° K-maps of four literals considered
 - Larger examples exist
- ° Don't care conditions help minimize functions
 - Output for don't cares are undefined
- ° Result of minimization is minimal sum-of-products
- ° Result contains prime implicants
- ° Essential prime implicants are required in the implementation